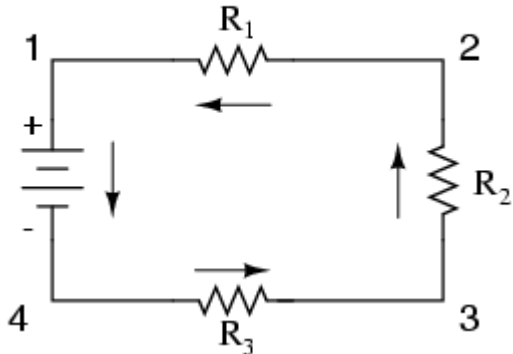
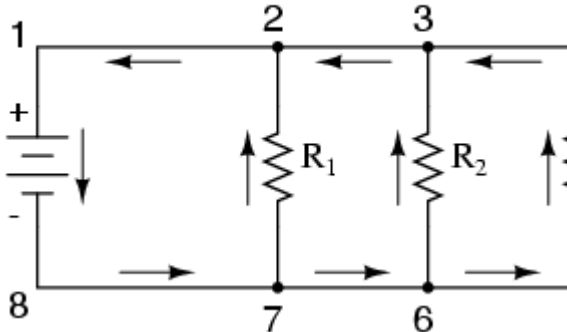


## Math-in-CTE Lesson Plan Template

Lesson Title: DC series and parallel circuits		Lesson # 13
Author(s): Jose A. Larrinaga	Phone Number(s):	E-mail Address(es):
	305-822-1500 ext 2415	<a href="mailto:jlarrinaga@dadeschools.net">jlarrinaga@dadeschools.net</a>
Juan M. Gonzalez	305-822-1500 ext 2452	
Occupational Area: Engineering Technology/Drafting		
CTE Concept(s): DC series and parallel circuits		
Math Concepts: Adding Fractions		
Lesson Objective: The student will be able to work with analyze series, parallel, and series -parallel DC circuits.		
Supplies Needed: paper, calculators, and optional computer stations		

<b>THE "7 ELEMENTS"</b>	<b>TEACHER NOTES (and answer key)</b>
<p><b>1. Introduce the CTE lesson.</b></p> <p><b>Lesson induction questions:</b></p> <p><b>Through question probing, assess students' math awareness as it relates to CTE topic.</b></p> <p><b>Why is it that in Christmas Tree when one light bulb in the wire does not work the rest of lights in that wire do not work either?</b></p> <p><b>Vocabulary: amperes, circuit, current, ohms, parallel, resistor, series, volts, voltage source, watts, wire</b></p>	<ol style="list-style-type: none"> <li>1. Amperes(A): a unit of electric currents</li> <li>2. Circuit: The conducting part, or a system of conducting parts, through which an electrical current passes.</li> <li>3. Current (I): The transfer of an electric charge through a material. Current is measured in amperes.</li> <li>4. Ohm (<math>\Omega</math>) : A unit of resistance.</li> <li>5. Parallel circuit: A method of connecting a circuit so that the current has two or more paths to follow.</li> <li>6. Resistor: A device that opposes the flow of an electric current. It is used for protection operation or current control.</li> <li>7. Series circuit: A method of connecting a circuit so that the current has one path to flow.</li> <li>8. Volt (V): A unit of electrical potential or pressure.</li> <li>9. Voltage (E): The electromotive force or electrical pressure. It is expressed in volts.</li> <li>10. Watts (W): A unit of power.</li> <li>11. Wire: A metal chord that connects electrical components.</li> </ol>

<p><b>2. Assess students' math awareness as it relates to the CTE lesson.</b></p> <p>How do you add and divide fractions?</p>	<p><a href="#">FRACTIONS QUIZ.doc</a></p>
<p><b>3. Work through the math example <i>embedded</i> in the CTE lesson.</b></p>	<p><a href="#">The Series Circuit.mht</a></p> <p><a href="#">Batteries and Bulbs as DC Circuit Example.mht</a></p> <p>Students will transform circuit formulas to obtain parallel and series circuits results.</p>
<p><b>4. Work through <i>related, contextual</i> math-in-CTE examples.</b></p> <p><math>R_T = R_1 + R_2 + R_3 + \dots + R_L</math></p> <p>T= total resistance</p> <p>L = Last resistor</p> <p><math>R_p = 1/R_1 + 1/R_2 + 1/R_3 + \dots + R</math></p>	<p><a href="#">file 13 information CTE\Electrical Circuits - Series and Parallel Circuits, Ohms Law.mht</a></p> <p style="text-align: center;"><i>Series</i></p>  <p style="text-align: center;"><i>Parallel</i></p> 

<p><b>5. Work through <i>traditional math</i> examples.</b></p> <p><b>See attached document Fraction Addition and Division.doc.</b></p>	<p><a href="#">Fraction Addition and Division.doc</a></p>
<p><b>6. Students demonstrate their understanding.</b></p>	<p>The students will demonstrate that they will be able to calculate the equivalent resistance of series and parallel circuits by mastering the basic arithmetic of fraction addition and division</p>
<p><b>7. Formal assessment.</b></p> <p><b>The format assessment will include in CTE series and parallel circuits.</b></p>	<p><a href="#">Series and Parallel Quiz.doc</a></p>

Student Name: \_\_\_\_\_ Period: \_\_\_\_\_ Date: \_\_\_\_\_

DC series and parallel series **answers to math examples**

Add the following fractions and simplify:

1)  $1/3 + 2/3 =$

2)  $2/5 + 1/5 =$

3)  $1/6 + 2/6 =$

Find the least common multiple for the following pairs of numbers:

4) 2:

4:

5) 2:

3:

6) 6:

8:

Find the least common denominators, then add and reduce the fractions:

7)  $2/4 + 1/2 =$

8)  $3/2 + 2/3 =$

9)  $3/8 + 5/6 =$

Divide and simplify

10)  $2/3 \div 1/6 =$

11)  $1 \div 2/5 =$

12)  $1 \div (1/2 + 1/3) =$

Student Name: \_\_\_\_\_ Period: \_\_\_\_\_ Date: \_\_\_\_\_

DC series and parallel series **answers to math examples**

1) 1

2)  $\frac{3}{5}$

3)  $\frac{1}{2}$

4) 4

5) 6

6) 24

7) 1

8)  $\frac{13}{6}$

9)  $\frac{58}{24} = \frac{29}{12}$

10) 4

11)  $\frac{5}{2}$

12)  $\frac{6}{5}$

Student Name: \_\_\_\_\_ Period: \_\_\_\_\_ Date: \_\_\_\_\_

DC series and parallel series **answers to math examples**

Add the following fractions and simplify:

1)  $\frac{1}{3} + \frac{2}{3} =$

2)  $\frac{2}{5} + \frac{1}{5} =$

3)  $\frac{1}{6} + \frac{2}{6} =$

Find the least common multiple for the following pairs of numbers:

4) 2:

4:

5) 2:

3:

6) 6:

8:

Find the least common denominators, then add and reduce the fractions:

7)  $\frac{2}{4} + \frac{1}{2} =$

8)  $\frac{3}{2} + \frac{2}{3} =$

9)  $\frac{3}{8} + \frac{5}{6} =$

Student Name: \_\_\_\_\_ Period: \_\_\_\_\_ Date: \_\_\_\_\_

DC series and parallel series **answers to math examples**

1) 1

2)  $\frac{3}{5}$

3)  $1 / 2$

4) 4

5) 6

6) 24

7) 1

8)  $\frac{13}{6}$

9)  $\frac{58}{24} = \frac{29}{12}$

## FRACTIONS QUIZ

### Add and simplify

1)  $\frac{1}{3} + \frac{5}{3} =$

2)  $\frac{5}{4} + \frac{3}{2} =$

3)  $\frac{5}{3} + \frac{7}{2} =$

4)  $\frac{1}{6} + \frac{1}{8} =$

### Divide and simplify

5)  $\frac{1}{5} \div \frac{3}{10} =$

6)  $1 \div \frac{2}{7} =$



## FRACTIONS QUIZ

### ANSWERS:

1) 2

2)  $11/4$

3)  $31/6$

4)  $7/12$


5)  $2/3$

6)  $7/2$

Student Name: \_\_\_\_\_ Period: \_\_\_\_\_ Date: \_\_\_\_\_

### Series and Parallel Circuit Quiz

Example

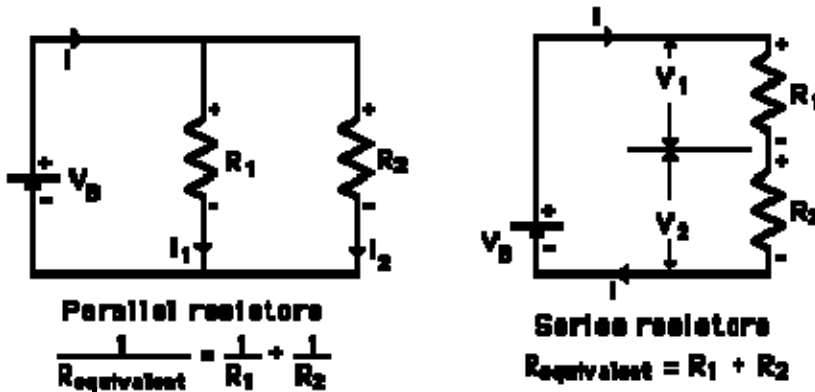

1. If in the series circuit  $R_1 = 10 \Omega$  and  $R_2 = 10 \Omega$ . What is  $R_{\text{equivalent}}$  ?
2. If in the series circuit  $R_1 = 1000 \Omega$  and  $R_2 = 0 \Omega$ . What is  $R_{\text{equivalent}}$  ?
3. If in the series circuit  $R_1 = 150 \Omega$  and  $R_2 = 200 \Omega$ . What is  $R_{\text{equivalent}}$  ?
4. If in the series circuit  $R_1 = 1 \text{ k} \Omega$  and  $R_2 = 10 \Omega$ . What is  $R_{\text{equivalent}}$  ?
5. If in the series circuit  $R_1 = 189 \Omega$  and  $R_2 = 234 \Omega$ . What is  $R_{\text{equivalent}}$  ?
6. If in the parallel circuit  $R_1 = 100 \Omega$  and  $R_2 = 100 \Omega$ . What is  $R_{\text{equivalent}}$  ?
7. If in the parallel circuit  $R_1 = 200 \Omega$  and  $R_2 = 300 \Omega$ . What is  $R_{\text{equivalent}}$  ?
8. If in the parallel circuit  $R_1 = 1 \text{ k} \Omega$  and  $R_2 = 2 \text{ k} \Omega$ . What is  $R_{\text{equivalent}}$  ?
9. If in the parallel circuit  $R_1 = 1 \text{ k} \Omega$  and  $R_2 = 5 \Omega$ . What is  $R_{\text{equivalent}}$  ?
10. If in the parallel circuit  $R_1 = 5 \Omega$  and  $R_2 = 600 \Omega$ . What is  $R_{\text{equivalent}}$  ?

Student Name: \_\_\_\_\_ Period: \_\_\_\_\_ Date: \_\_\_\_\_  
Series and Parallel Circuit Quiz

Answer Sheet

1.  $20 \Omega$

2.  $1000 \Omega$  or  $1 \text{ k} \Omega$

3.  $350 \Omega$

4.  $1010 \Omega$

5.  $423 \Omega$

6.  $50 \Omega$

7.  $120 \Omega$

8.  $2000/3 \Omega$  or  $\approx 666.67 \Omega$

9.  $1000/201 \Omega$  or  $\approx 4.98 \Omega$

10.  $600/121 \Omega$  or  $\approx 4.96 \Omega$